

5.1.57. feladat

$$q = 2$$

$$y_h = 5$$

5. ASZINKRON GÉPEK

5.2. Egyfázisú aszinkron motorok

5.2.1. feladat

$$a) I_s = \frac{P_s}{U \cdot \cos \varphi_s} = \frac{1400}{220 \cdot 0,8} = 7,95 \text{ A}$$

$$b) Z_s = \frac{U}{I_s} = \frac{220}{7,95} = 27,67 \Omega$$

$$R_s = Z_s \cdot \cos \varphi_s = 27,67 \cdot 0,8 = 22,14 \Omega$$

$$X_s = Z_s \cdot \sin \varphi_s = 27,67 \cdot 0,6 = 16,60 \Omega$$

$$\varphi_s = 36,86^\circ$$

$$c) X_c = \frac{1}{\omega \cdot C} = \frac{10^6}{314 \cdot 30} = 106,16 \Omega$$

$$d) Z_s = \sqrt{R_s^2 + (X_c - X_s)^2} = \sqrt{(22,14)^2 + (106,16 - 16,60)^2} \approx 92,25 \Omega$$

$$I_s = \frac{U}{Z_s} = \frac{220}{92,25} \approx 2,38 \text{ A}$$

$$\cos \varphi_{s'} = \frac{R_s}{Z_{s'}} = \frac{22,14}{92,25} = 0,24$$

$$\varphi_{s'} = 76,12^\circ$$

$$e) I_{cp} = \frac{U}{X_c} = \frac{220}{106,16} = 2,07 \text{ A}$$

$$\Delta I_c = I_s - I_{cp} = 2,38 - 2,07 = 0,31 \text{ A}$$

Az árama 0,31 A-rel csökken.

a) A főfázis fázisszöge:

$$\cos \varphi_f = \frac{R_f}{Z_f} = \frac{30}{40} = 0,75$$

$$\varphi_f = \arccos \varphi_f = 41,4^\circ$$

b) A főfázis árama:

$$I_f = \frac{U}{Z_f} = \frac{220}{40} = 5,5 \text{ A}$$

c) A segéd fázis teljesítménytényezője:

$$\varphi'_s = 90^\circ - \varphi_f = 48,6^\circ \quad \cos \varphi'_s = 0,66$$

$$I_s = 7,95 \text{ A}$$

$$Z_s = 27,67 \Omega$$

$$R_s = 22,14 \Omega$$

$$X_s = 16,60 \Omega$$

$$X_c = 106,16 \Omega$$

$$I_s = 2,38 \text{ A}$$

$$\cos \varphi_{s'} = 0,24$$

$$\Delta I_c = 0,31 \text{ A}$$

5.2.2. feladat

$$\cos \varphi_f = 0,75^\circ$$

$$\varphi_f = 41,4^\circ$$

$$I_f = 5,5 \text{ A}$$

$$\cos \varphi'_s = 0,66$$