

7. FÁZISJAVÍTÁS

$$Q_{\dot{u}j} = \sqrt{S_e^2 - P_{\dot{u}j}^2} = \sqrt{79,88^2 - 75,89^2} = 24,93 \text{ kvar}$$

$$Q_{szűks} = Q_e - Q_{\dot{u}j} = 66 - 24,93 = 41,07 \text{ kvar}$$

$$d) C_{szűks} = \frac{Q_{szűks} \cdot 10^6}{3 \cdot U_v^2 \cdot \omega} = \frac{41,07 \cdot 10^3 \cdot 10^6}{3 \cdot 380^2 \cdot 314} = 301,93 \text{ } \mu\text{F}$$

$$\omega = 2 \cdot \pi \cdot f = 2 \cdot 3,14 \cdot 50 = 314 \text{ 1/s}$$

$$Q_{szűks} = 41,07 \text{ kvar}$$

$$C_{szűks} = 301,93 \text{ } \mu\text{F}$$

7.8. feladat

$$a) S_1 = \frac{P_{fel1}}{\cos \varphi_1} = \frac{25000}{0,777} = 32175 \text{ V} \cdot \text{A}$$

$$b) Q_1 = S_1 \cdot \sin \varphi_1 \quad \sin \varphi_1 = \sqrt{1 - \cos^2 \varphi_1} = \sqrt{1 - 0,777^2} = 0,6295$$

$$Q_1 = 32175 \cdot 0,6295 = 20254 \text{ var}$$

$$c) S_2 = \frac{P_{le2}}{\eta_2 \cdot \cos \varphi_2} = \frac{50000}{0,82 \cdot 0,791} = 77087 \text{ V} \cdot \text{A}$$

$$d) Q_2 = S_2 \cdot \sin \varphi_2 \quad \sin \varphi_2 = \sqrt{1 - \cos^2 \varphi_2} = \sqrt{1 - 0,791^2} = 0,6118$$

$$Q_2 = 77087 \cdot 0,6118 = 47163 \text{ var}$$

$$e) P_2 = \frac{P_{le2}}{\eta_2} = \frac{50000}{0,82} = 60976 \text{ W}$$

$$P_o = P_{fel1} + P_2 = 25000 + 60976 = 85976 \text{ W}$$

$$f) Q_o = Q_1 + Q_2 = 20254 + 47163 = 67417 \text{ var}$$

$$g) S_o = \sqrt{P_o^2 + Q_o^2} = \sqrt{85976^2 + 67417^2} = 109256 \text{ V} \cdot \text{A}$$

$$h) \cos \varphi = \frac{P_o}{S_o} = \frac{85956}{108961} = 0,7869$$

$$i) Q_{\dot{u}j} = P_o \cdot \tan \varphi' = 85976 \cdot 0,4843 = 41638 \text{ var}$$

$$j) Q_c = Q_o - Q_{\dot{u}j} = 67417 - 41638 = 25779 \text{ var}$$

$$k) C = \frac{Q_c}{2 \cdot \pi \cdot f \cdot U^2} = \frac{25298}{2 \cdot \pi \cdot 50 \cdot 380^2} = 5,68 \cdot 10^{-4} \text{ F} = 568 \text{ } \mu\text{F}$$

$$S_1 = 32,175 \text{ kV} \cdot \text{A}$$

$$Q_1 = 20,254 \text{ kvar}$$

$$S_2 = 77,087 \text{ kV} \cdot \text{A}$$

$$Q_2 = 47,163 \text{ kvar}$$

$$P_o = 85,976 \text{ kW}$$

$$Q_o = 67,417 \text{ kvar}$$

$$S_o = 109,256 \text{ kV} \cdot \text{A}$$

$$\cos \varphi = 0,7869$$

$$Q_{\dot{u}j} = 41,638 \text{ kvar}$$

$$Q_c = 25,779 \text{ kvar}$$

$$C = 568 \text{ } \mu\text{F}$$